
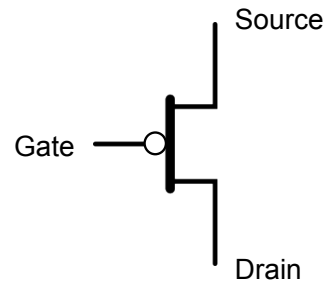



What is Digital

Transition from Analog → Digital


# Transistors

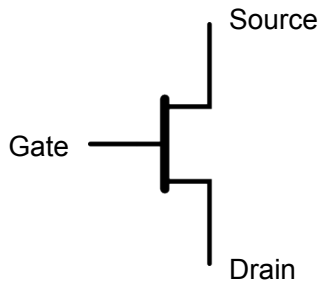


## Transistors - Digital Circuits

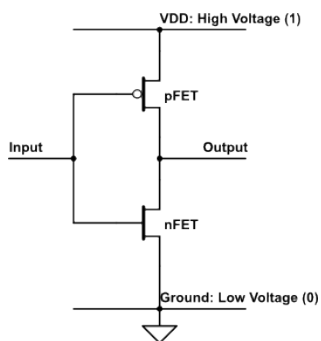

## Logic Gates

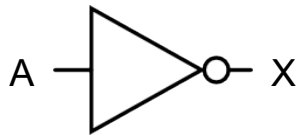


A	X

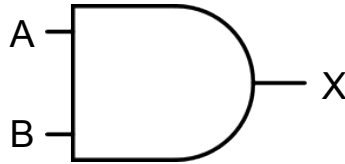


A	B	X

## Logic Gates


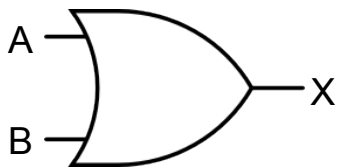


A	B	X

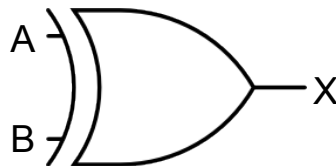


A	B	X


## Logic Gates

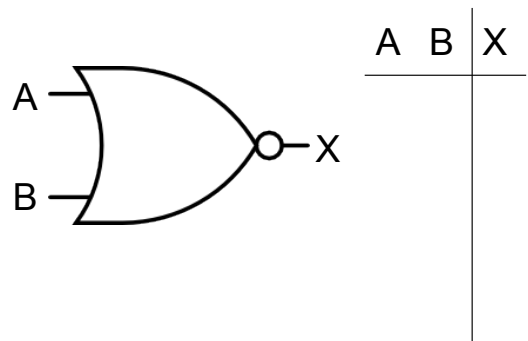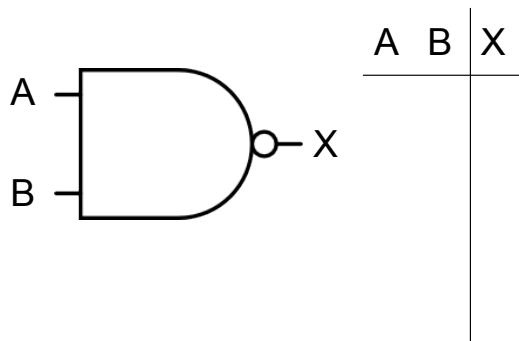

## Logic Gates

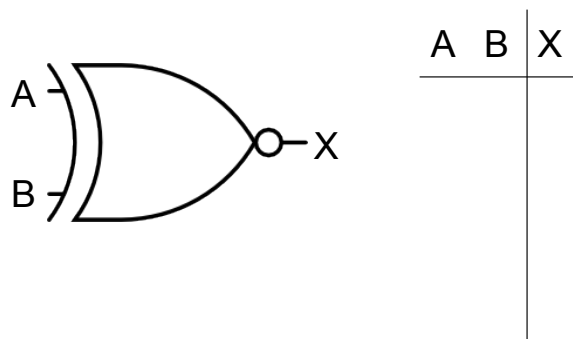

## Logic Gates


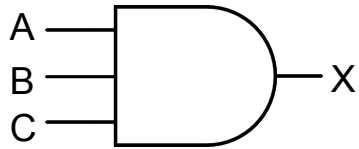


A	B	C	X
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


## Transistor Count

Gate	Transistors
NOT	
AND	
OR	
XOR	
NAND	
NOR	
XNOR	

## AND / OR Conversion

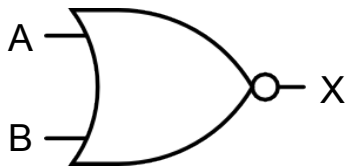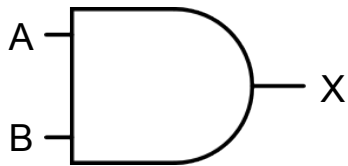


## Logic Circuits

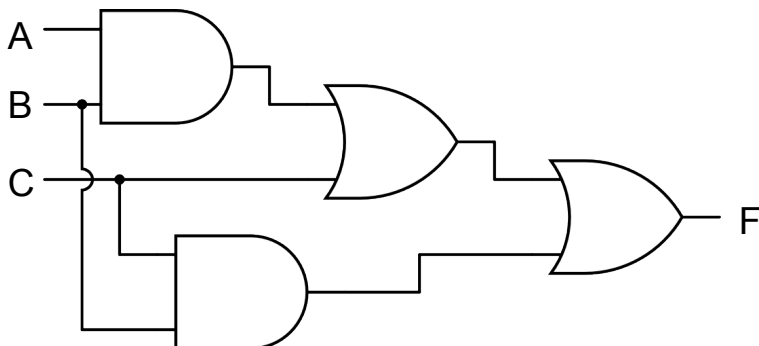

A	B	C	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

## Combine Inverters

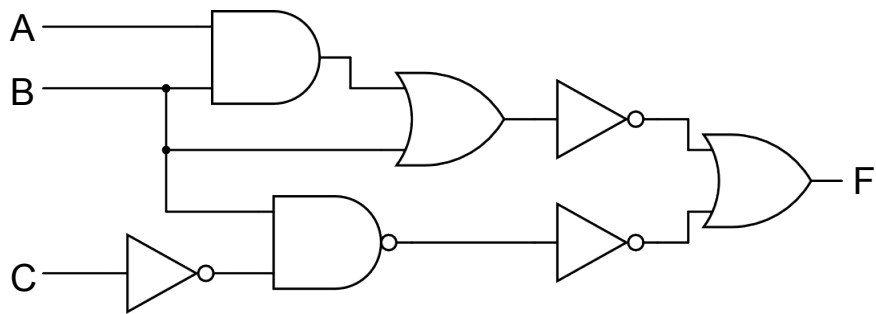

## Digital Circuits

## Combinational Circuits

## Digital Expressions




## Sum of Products (SOP)

## Sum of Products (SOP)

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Y =

## Sum of Products (SOP)

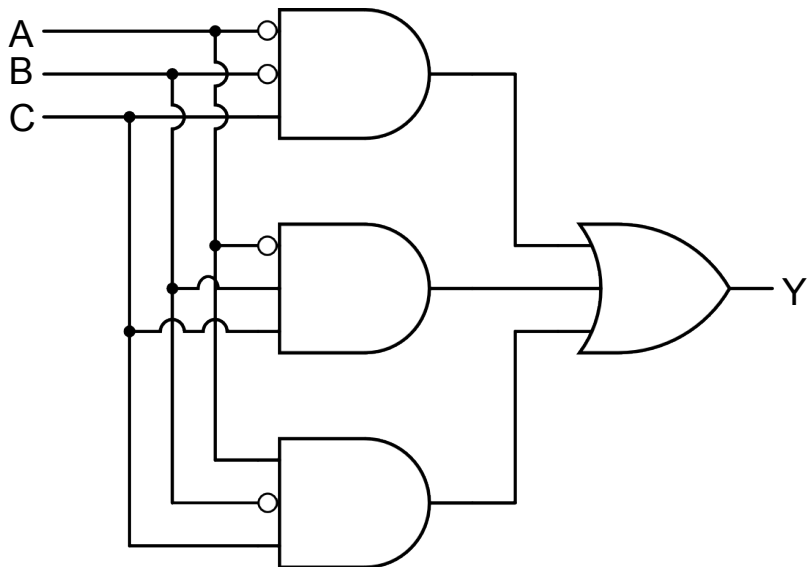


## Product of Sums (POS)

## Product of Sums (POS)

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Y =

## Product of Sums (POS)

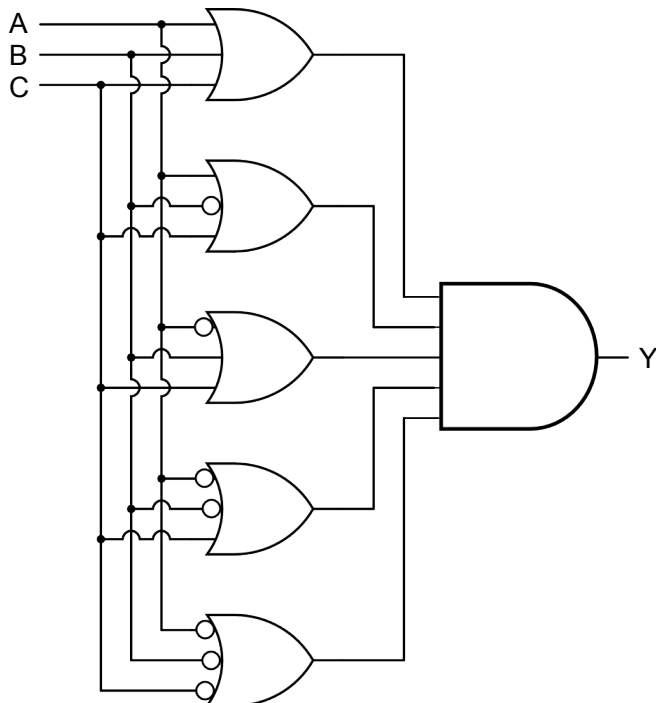

## Minterms / Maxterms

Term	ABC	Minterm	Maxterm	F
0	000			0
1	001			1
2	010			0
3	011			1
4	100			0
5	101			1
6	110			0
7	111			0

## SOP / POS Terms