 




Digital Memory Circuits

State Stability




Basic Memory Cell


Inputs	Outputs

  

SR NOR Cell

 

SR NAND Cell

 



Basic Memory Cell

NOR Memory Cell			
S	R	Q	QN
0	0		
0	1		
1	0		
1	1		

NAND Memory Cell			
S	R	Q	QN
0	0		
0	1		
1	0		
1	1		

D-Latch

D-Latch

  

D-Latch

D - Memory Cell


Latch vs Flip Flop

Clk




Reset Input


D - Flip Flop (DFF)

 


D	Q

 


JK - Flip Flop

 


J K	Q

 

T - Flip Flop

 

T	Q

 

Registers

